

Physics Challenges for Teachers and Students

* * *

Here we present the solutions to the March 2002 *Challenges*:

A Vacuum Squeezer

From the first law of thermodynamics,

$$dU = dQ - dW,$$

where dU is the change in the internal energy of the gas, dQ is the heat added to the gas, and dW is the work done by the gas.

For a monoatomic ideal gas

$$U = \frac{3}{2}nRT,$$

where n is the quantity of gas in moles, R is the universal gas constant, and T is the absolute temperature of the gas. For a fixed quantity of the gas

$$dU = \frac{3}{2}nR dT. \quad (1)$$

The work done by the expansion of the gas is

$$dW = P dV.$$

If the cross-section area of the piston is A , the spring constant k , and the distance from the left edge of the container to the piston x , then the volume of gas in the cylinder is

$$V = Ax \quad \text{and} \quad dV = A dx.$$

The force on the piston exerted by the spring is kx ; therefore, the pressure of the gas is

$$P = \frac{kx}{A} \quad \text{and} \quad dP = \frac{k dx}{A}.$$

From the ideal gas law:

$$PV = nRT \text{ or } d(PV) = d(nRT) \text{ or } P dV + V dP = nR dT.$$

Since $P dV = V dP = kx dx$, the ideal gas law can be written as

$$2P dV = nR dT$$

or

$$dW = PdV = (1/2)nRdT. \quad (2)$$

Substituting for dU and dW in the first law using Eq. (1) and Eq. (2):

$$\frac{3}{2}nR dT = dQ - \frac{1}{2}nR dT \quad \text{or} \quad dQ = 2nR dT.$$

The heat capacity of the system is then

$$C = \frac{dQ}{dT} \quad \text{or} \quad C = 2nR.$$

With the quantity of gas $n = 1$ mol,

$$C = (2 \text{ mol})R \approx 16.6 \text{ J/K}.$$

(Contributed by Richard Morra, Pascack Valley Regional HS District (Retired), Hillsdale, N.J.)

Futile resistance

Let V_1 be the voltage across the ammeter in the first circuit. In the second circuit, that voltage becomes $3V_1$ because the current triples. Similarly, the initial voltmeter reading can be denoted V_2 , and the final reading $V_2/3$. Since the battery remains in series with the ammeter, the battery current does not depend on the resistance distribution between the battery and the ammeter; for convenience, we can assume that the battery has zero resistance. Then the voltage across the battery remains 6 V, so:


$$V_1 + V_2 = 6$$

$$3V_1 + (V_2/3) = 6,$$


and $V_2 = 4.5 \text{ V}.$

(Contributed by Christina Domnisoru, a junior at Maine School of Science and Mathematics, Limestone, Maine)

Red Square

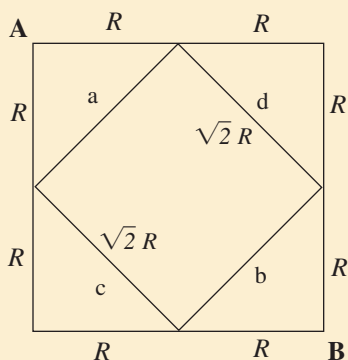

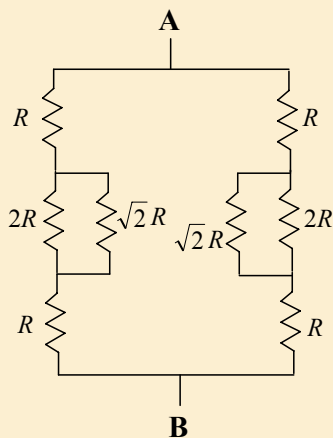By symmetry, wires a and b each have no potential difference between their ends. Thus, no current flows through these wires and they may be removed. Assuming that the half-side of the large square has a resistance of $R = \frac{\rho d}{2}$, the circuit reduces to the following:



The resistance of the left side is

$$2R + \frac{2R \cdot \sqrt{2}R}{2R + \sqrt{2}R} = 2R + \frac{2\sqrt{2}}{2 + \sqrt{2}} R = 2\sqrt{2}R.$$

Meanwhile, the right side has the same resistance, so the resistance between points A and B

$$\text{is } \sqrt{2}R = \frac{\sqrt{2}}{2} \rho d.$$

(Contributed by Gary Johnson, Michigan Lutheran Seminary, Saginaw, Mich.)

Several other readers also submitted correct solutions for this issue. We wish to thank and recognize these contributors:

Mike Faleski, Maine School of Science and Mathematics, Limestone, Maine

Carl E. Mungan, U.S. Naval Academy, Annapolis, Md.

Inge H. A. Pettersen, St. Olav High School, Stavanger, Norway

Nunzio Thron, a senior at Maine School of Science and Mathematics, Limestone, Maine

Reza Vafabakhsh, a student at the Institute for Advanced Studies in Basic Science, Zanjan, Iran

Clarke Wellborn and his students, Brevard College, Brevard, N.C.

Please send correspondence to:

Boris Korsunsky
Weston High School
444 Wellesley St.
Weston, MA 02493-2631;
korsunbo@gse.harvard.edu